

Proper Wiring of AO3 Option A/D Converter

Getting started:

This technical note will demonstrate how to properly wire your AO3 card to prevent signal drift.

The important element to note is that the negative channel needs to be attached to GROUND on the Eason unit, and that your cable shield should be referenced to a true earth ground. (Not the Eason GND connection)

The setup: